


Induction Exercises

Ben Kettle - Adapted from MIT 8.02

22 January 2020

1 Falling Loop

Suppose a rectangular loop with mass m , width w , vertical length l , and resistance R is falling out of a magnetic field under the influence of gravity. The magnetic field is uniform and out of the page ($\vec{B} = B\hat{x}$) within the area shown and zero outside of that area. The loop is exiting the magnetic field with $\vec{V}(t) = V(t)\hat{z}$, where $V(t) < 0$ (the loop is moving downward). Define the distance from the top of the loop to the bottom of the magnetic field at time t as $z(t)$.

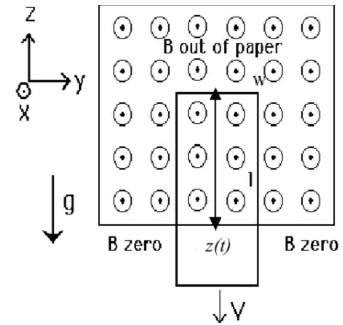

- What is the relationship between the distance $z(t)$ and the speed $V(t)$? Remember that $z(t)$ is positive and decreasing in time, and $V(t)$ is negative.
- If we define the area vector \vec{A} to be out of the page, what is the magnetic flux Φ_B through the circuit at time t (in terms of $z(t)$, not $V(t)$).
- Find $d\Phi_B/dt$. Is it positive or negative at time t ? Your answer should include $V(t)$.
- What is the direction of the induced current in the loop?
- What is the direction of the magnetic field created by this current?
- What is the magnitude of the current flowing in the circuit at the time t ?
- What other force (besides gravity) is acting on the loop in the $\pm\hat{z}$ direction? Give the magnitude and direction of this force in terms of the quantities given.
- Assume the loop has reached terminal velocity—it is no longer accelerating. What is the magnitude of that terminal velocity in terms of the given quantities?

2 Power Transmission

You've started a new job at the electric company, and want to determine the best way to send power across Ancona. The stretch of power lines you are working with has a total resistance of $.40\Omega$, and the solar panels you are using as a power source generate $240V$ power. On average, $120kW$ of power is sent through the lines. You are considering using a transformer, and want to minimize power loss during transmission.


- (a) Calculate the power loss over the length of the transmission lines without the transformer.
- (b) Calculate the power loss through the transmission lines with a transformer added between the solar panels and the transmission lines. The transformer has 10 primary (input) turns and 1,000 secondary (output) turns.
- (c) Should you use the transformer in this case? How could you decrease power loss further?

3 Circuit Concepts

A circuit consists of two resistors R_1 and R_2 , a capacitor, and a switch. The switch has been open for a very long time and is closed at $t = 0$.

1. What is the current through the capacitor at $t = 0^+$, just after the switch is closed?
2. What are the currents through R_1 and R_2 at $t = 0^+$?
3. What is the current through the capacitor at $t = \infty$?
4. What are the currents through R_1 and R_2 at $t = \infty$?


4 Purely Resistive Circuit

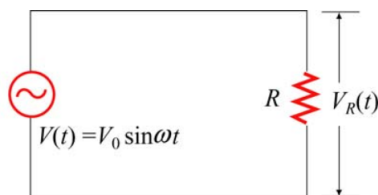

Recall that for AC Circuits, we define $V(t) = V_0 \sin(\omega t)$ and $I(t) = I_0 \sin(\omega t - \phi)$. The above circuit consists of an AC voltage source with voltage defined by $V(t) = V_0 \sin(\omega t)$ and a resistor with resistance R .

- (a) Use Kirchoff's loop rule to find the circuit equation.
- (b) Find the values of I_0 and ϕ for this circuit.
- (c) Find the room-mean-squared power P_{rms} dissipated by this circuit. Recall that $\frac{1}{T} \int_0^T \sin^2(t) dt = \frac{1}{2}$.


5 Purely Inductive Circuit

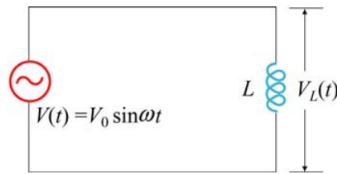

Now, the same voltage source with $V(t) = V_0 \sin(\omega t)$ is connected to an inductor with inductance L .

- (a) Use Kirchoff's loop rule to find the circuit equation.
- (b) For current in the form $I(t) = I_0 \sin(\omega t - \phi)$, find the values of I_0 and ϕ for this circuit.

6 Purely Capacitive Circuit

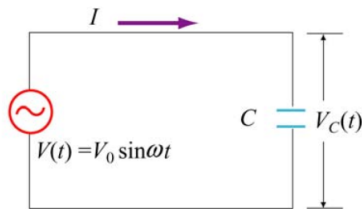

Finally, the same voltage source is connected to only a capacitor. Once again, voltage is given by $V(t) = V_0 \sin(\omega t)$.

- (a) Use Kirchoff's loop rule to find the circuit equation.
- (b) For current in the form $I(t) = I_0 \sin(\omega t - \phi)$, find the values of I_0 and ϕ for this circuit.